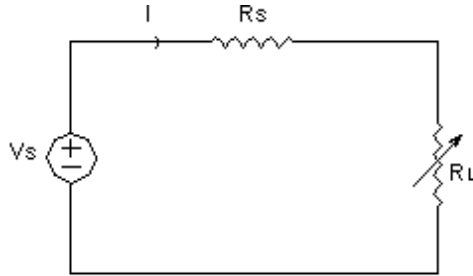


CONDITION FOR MAXIMUM POWER AND MAXIMUM REACTIVE POWER

I. CONDITION FOR MAXIMUM POWER:

The maximum power transfer theorem states that maximum power will be delivered to that load resistance R_L for which $R_L = R_S$ driven by an independent voltage source having a series resistance R_S .

Let us consider a circuit given below:



For this circuit the power absorbed by the load resistance ' R_L ' is, $P_L = I^2 R_L$ where $I = V_S / (R_S + R_L)$

$$\therefore P_L = \left(\frac{V_S}{R_S + R_L} \right)^2 R_L = V_S^2 \cdot \frac{R_L}{(R_S + R_L)^2}$$

To get the condition for this power to be maximum, differentiate P_L w.r.t. ' R_L ' and equate it to zero.

$$\text{i.e. } \frac{dP_L}{dR_L} = 0 \Rightarrow \frac{d}{dR_L} \left[V_S^2 \frac{R_L}{(R_S + R_L)^2} \right] = 0$$


$$\Rightarrow \frac{V_S^2 \left[(R_S + R_L)^2 \cdot 1 - R_L \cdot 2(R_S + R_L) \right]}{(R_S + R_L)^4} = 0$$

$$\Rightarrow \left[(R_S + R_L)^2 \cdot 1 - R_L \cdot 2(R_S + R_L) \right] = 0$$

$$\Rightarrow (R_S + R_L) - 2R_L = 0$$

$$\boxed{R_L = R_S} \quad \text{and } P_{L \max} = \frac{V_S^2}{4R_S} \text{ watts.}$$

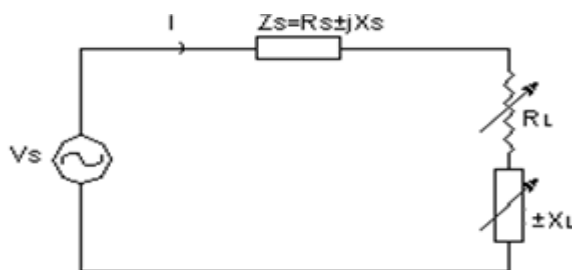Now consider the most interesting A/c circuit given below:



Z_s = Source internal impedance;

R_s = source internal resistance;

X_s = source internal reactance and it could be *either inductive reactance or capacitive reactance*;

Z_L = Load impedance;

R_L = Load resistance;

X_L = Load reactance and it could be *either load inductive reactance or load capacitive reactance*;

To obtain the condition for power transfer, let us analyze the following cases:

Case-1: If both R_L and X_L are variable.


We know that $P_L = I^2 \cdot R_L$

By looking at the given circuit one can easily confirm that the condition for maximum P_L is

$$\boxed{R_L = R_s} \quad \text{and} \quad \boxed{X_L = X_s^*} \quad \text{i.e., } X_L \text{ is the conjugate of } X_s.$$

Thus, if $\boxed{Z_L = Z_s^*}$ i.e., if Z_L is the complex conjugate of Z_s then, the power transferred to the load will be maximum.

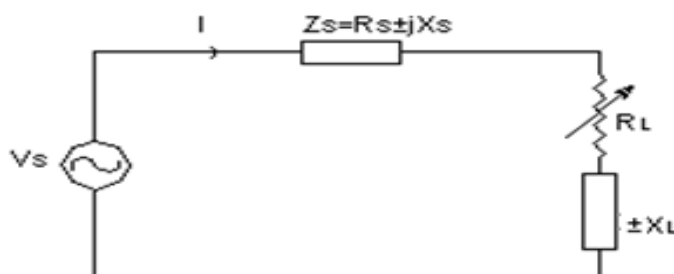Case-2: If only R_L is variable and X_L is constant.



$$P_L = I^2 R_L = \left(\frac{V_s}{Z}\right)^2 \cdot R_L; \quad \text{where } \bar{Z} = \bar{R}_L + \bar{Z}_1; \quad \text{and } Z_1 = (R_s + j(X_s + X_L))$$

Proof:


$$P_L = \left(\frac{V_s}{Z}\right)^2 R_L = V_s^2 \left(\frac{R_L}{(R_L + Z_1)^2}\right).$$

$$\therefore \frac{dP_L}{dR_L} = 0 \Rightarrow \frac{V_s^2 \left[(R_L + Z_1)^2 \cdot 1 - R_L \cdot 2(R_L + Z_1) \right]}{(R_L + Z_1)^4} = 0$$

$$\Rightarrow (R_L + Z_1)^2 - 2R_L (R_L + Z_1) = 0 \quad \Rightarrow (R_L + Z_1) = 2R_L \Rightarrow R_L = |Z_1|.$$

Therefore, the condition for P_L max, $R_L = |Z_1|$.

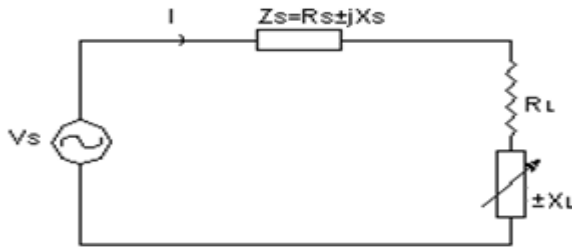Case-3: Only X_L is variable and R_L is constant



$$P_L = I^2 R_L \text{ where } I = \frac{V_s}{(R_s + R_L) + j(X_s + X_L)}.$$

Then, P_L will be max, when I is max. i.e. when $X_L = X_s^*$ for a given R_L .

II. CONDITION FOR MAXIMUM REACTIVE POWER:

For the above circuit the reactive power consumed by the load is given by $Q_L = I^2 \cdot X_L$.

$$\text{where } I = \frac{V_s}{(R_s + R_L) + j(X_s + X_L)}$$

$$\therefore Q_L = \left(\frac{V_s}{Z}\right)^2 X_L; \quad Z = Z_1 + jX_L; \quad \text{where } Z_1 = ((R_s + R_L) + jX_s)$$

The condition for Q_L max. is obtained by calculating $\frac{dQ_L}{dX_L} = 0$, which yields $X_L = |Z_1|$ with the sign of the X_L opposite to that of X_s .

As an example, with $V_s = 400$ V; $R_s = 30$ ohms; $X_s = 20$ ohms (inductive reactance); $R_L = 25$ ohms; the values obtained are $Q_{L \text{ max}} = -2076.65$ Reactive VA (capacitive) and the corresponding $X_L = -58.52$ ohms (capacitive reactance).

